

2.45 GHz T/R, RF switch for e.g. bluetooth application using PIN diodes

1 Introduction.

One of the most important building blocks for today’s wireless communication equipment is a high performance RF switch. The switch main function is to switch an RF port (ANT) between the transmitter (TX) and the receiver (RX). The most important design requirements are, Low insertion Loss (IL), Low intermodulation distortion, (IMD), High isolation between TX and RX, Fast switching and Low current consumption especially for portable communication equipment. This application note addresses a transmit and receive switch for 2.4-2.5 GHz the unlicensed ISM band, in which e.g. the bluetooth standard operates. The design demonstrates a high performance T-R switch utilising low cost Philips BAP51-02 PIN Diodes as switching elements.

2 PIN diode switch design.

There are a number of PIN diode based, single pole double throw (SPDT) topologies, which are shown in the figures 1,2 and 3. All these topologies are being used widely in RF and microwave design. They all will give good performance, due to their symmetry they will show the same performance in both the RX and TX mode. The disadvantage of these topologies is the need of a pair of digital control signals, and in both TX and RX mode bias current is needed.

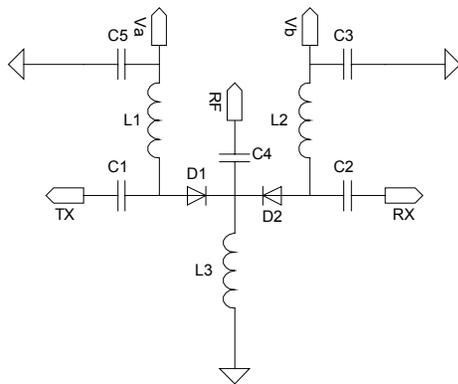


Figure 1. SPDT switch with series diodes

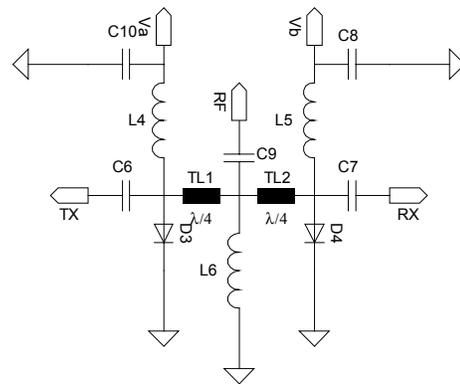


Figure 2. SPDT switch with $\lambda/4$ sections to permit shunt diodes

The topology we used for the design in this application note is shown in fig 4. Typically this is a combination of figure 1 and 2. The design consists of a series-connected PIN diode, placed between the transmitter-amplifier and antenna, and a shunt-connected PIN diode at the receiver-port, which is a quarter wavelength away from the antenna. In the transmit-mode both diodes are biased with a forward bias current. Both diodes are in the low impedance state. Which means a low-loss TX-ANT path and a protected RX port from the TX power.

The $\lambda/4$ transmission line transforms the low impedance at the RX port to a high impedance at the antenna. In the receive mode both diodes are zero biased (high impedance state), which results in a low loss path between antenna and receiver and high isolation ANT-TX path. One of the advantages of this approach is no current consumption is needed in the receive mode.

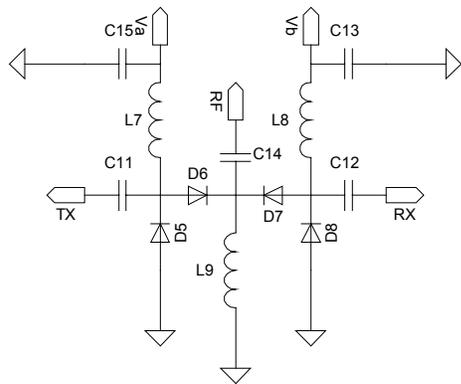


Figure 3. SPDT switch with series shunt diodes which results in high isolation

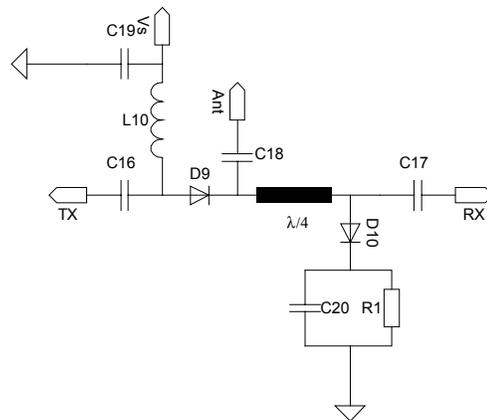


Figure 4. SPDT switch with a combination of a series and a shunt connected PIN diode.

The PIN diodes used in an switch like this should have low capacitance at zero bias ($V_R=0V$), and low series resistance at low forward current. The BAP51-02 typical shows $0.4pF@0V;freq=1MHz$ and $2 \Omega @3mA;freq=100MHz$. For the shunt diode also low series inductance is required, for the BAP51-02 this is $0.6 nH$.

3 Circuit design.

Circuit and Layout has been designed with the use of Agilent’s Advance Design System (ADS). The target performance of the switch is shown in table 1.

| Mode | RX (0V) | TX(3mA) |
|---------------------|-----------|------------|
| Insertion Loss | < 0.65 dB | < 0.8 dB |
| Isolation TX/RX | >18 dB | >14.5 dB |
| Isolation RX/Ant | >16.5 | - |
| Isolation TX/Ant | - | >14.5dB |
| VSWR RX | <1.2 | - |
| VSWR TX | | <1.3 |
| VSWR Ant | <1.2 | <1.3 |
| Power handling | +20dBm | +20dBm |
| Current consumption | | 3mA @ 3.7V |

Table 1

The ADS circuit of the switch is given in figure 5. Notice that D1 is the series connected PIN diode in the receive path en D2 is connected in shunt in the receive RF path. DC bias current is provided through inductance L1, and limited to about 3mA by resistor R1=680 Ω . Notice also that the $\lambda/4$ microstripline (width 1.136mm, length =16.57mm) is divided into several sections in order to save some board space. All the footprints for the SMD components have been modelled as a gap and a piece of stripline in order to approach the actual practice of the design on PCB.

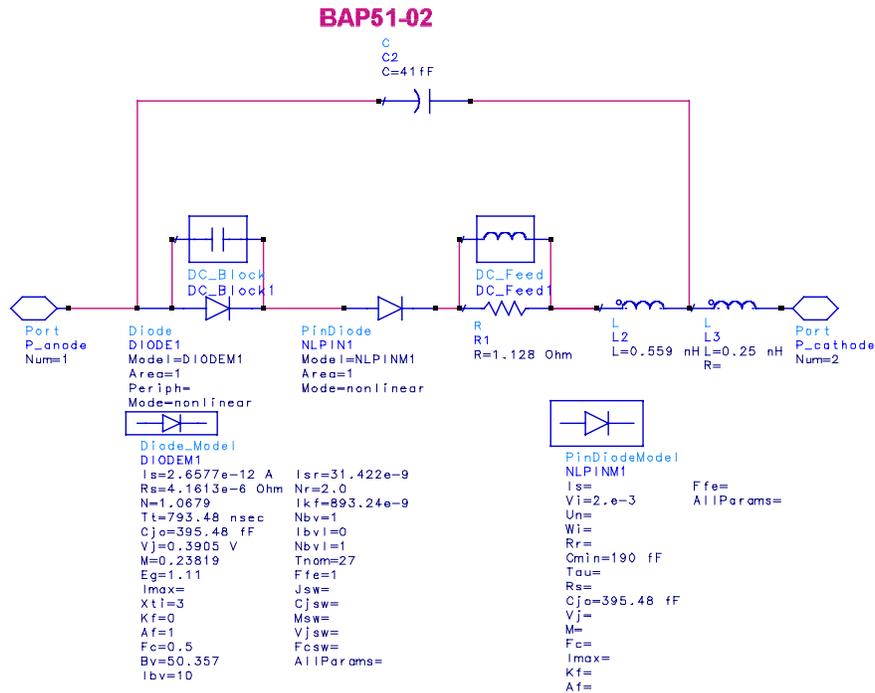


Figure 6; BAP51-02 Small Signal Model for an ADS environment

5 Circuit and Layout Description

The circuit diagram for the switch is shown in figure 7 and the PC board layout is shown in figure 8. The bill of materials for the switch is given in table 2.

For the PC board 0.635mm thick FR4 material ($\epsilon_r = 4.6$) metalized on two sides with 35 μm thick copper, 3 μm gold plated was used. On the test board SMA connectors were used to feed the RF signals to the design.

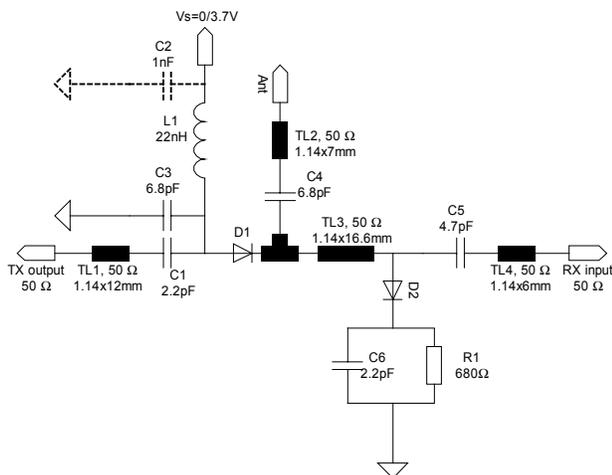


Figure 7; circuit diagram

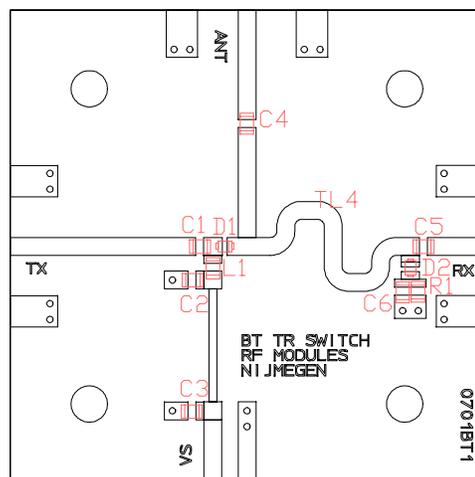


Figure 8; PC board Layout.

| Component | Value | Footprint | Manufacturer |
|-----------|--------|-----------|--------------|
| C1 | 2.2 pF | 0402 | Philips |
| C2 | 1 nF | 0402 | Philips |

| | | | |
|-----|------------------------|------|-------------|
| C3 | 6.8 pF | 0402 | Philips |
| C4 | 6.8 pF | 0402 | Philips |
| C5 | 4.7 pF | 0402 | Philips |
| C6 | 2.2 pF | 0402 | Philips |
| R1 | 680 Ω | 0402 | Philips |
| D1 | BAP51-02 | SC79 | Philips |
| D2 | BAP51-02 | SC79 | Philips |
| L1 | 22 nH | 1005 | Taiyo yuden |
| TL1 | $\lambda/4; 50 \Omega$ | | on the PCB |

Table 2 Bill of materials *C2 is optional.

6 Measurement results.

In table 3 the measured performance of the switch is summarised. In figure 9, both the simulation and Measurement results in TX mode (3.7V/3mA) is shown, for the RX mode this can be seen in fig.10.

| parameter | Mode | |
|---|-----------|------------|
| | RX (0V) | TX(3mA) |
| Insertion Loss @ 2.45GHz | < 0.57 dB | < 1.0 dB |
| Isolation TX/RX @ 2.45GHz | >20.4 dB | >23.6 dB |
| Isolation Ant/RX @ 2.45 GHz | - | >23.5 dB |
| Isolation TX/Ant @2.45 GHz | >19.76 dB | - |
| VSWR RX @2.45 GHz | 1.24 | - |
| VSWR TX @2.45 GHz | - | 1.35 |
| VSWR Ant @2.45 GHz | 1.19 | 1.29 |
| IM3 Pin 0 dBm f1=2.449 GHz f2=2.451 GHz | +39 dBm | +40 dBm |
| IP3 Pin 0 dBm f1=2.449 GHz f2=2.451 GHz | +43.8 dBm | +44.8 dBm |
| IM3 Pin +20 dBm f1=2.449 GHz f2=2.451 GHz | +38.5 dBm | +39.5 dBm |
| IP3 Pin +20 dBm f1=2.449 GHz f2=2.451 GHz | +43.3 dBm | +44.3 dBm |
| Power handling | +20 dBm | +20 dBm |
| Current consumption | | 3mA @ 3.7V |

Table 3 measured switch performance.

Intermodulation distortion measurements were performed as follows. In both RX and TX state, first the measurements were done with two input-signals, each at 0 dBm and second each signal at +20 dBm. In transmit state these signals were applied to the TX port, distortion was measured at the antenna port, while the RX port was terminated with 50 Ω . In receive state the two signals were applied to the ANT port, distortion was measured at the RX port, with the TX port terminated.

According to reference 2, the third order harmonic distortion product is 9.54 dB less than the third order Intermodulation product, the third order harmonic intercept point IP3 is 9.54/2 higher than the third order Intermodulation intercept point IM3.

simulation and measurement results in transmit mode Is=3mA

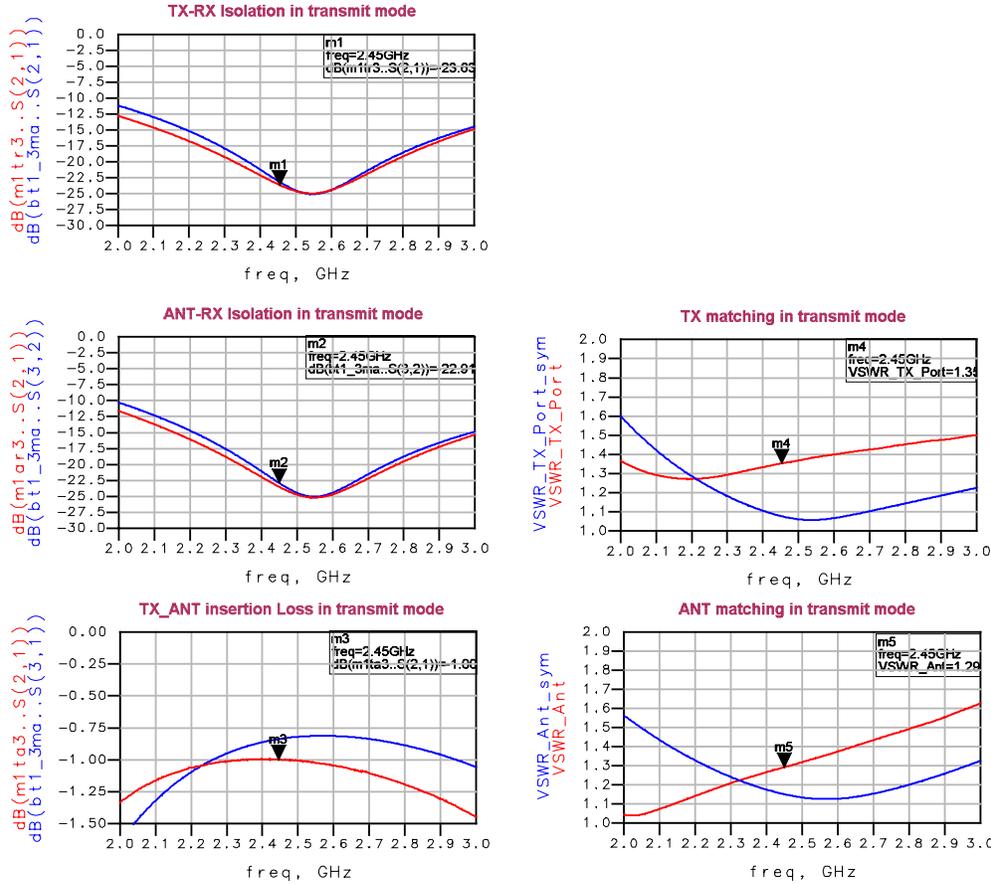


Figure 9; Results in TX mode; red curves are measurements, blue curves are the simulated ones.

Remark: Loss and Isolation results are all including approximately 0.2 dB loss of the SMA connectors which were used to feed the RF signals through the design. this has a great effect on the Insertion-Loss results.

simulation and measurement results in receive mode Vs=0V

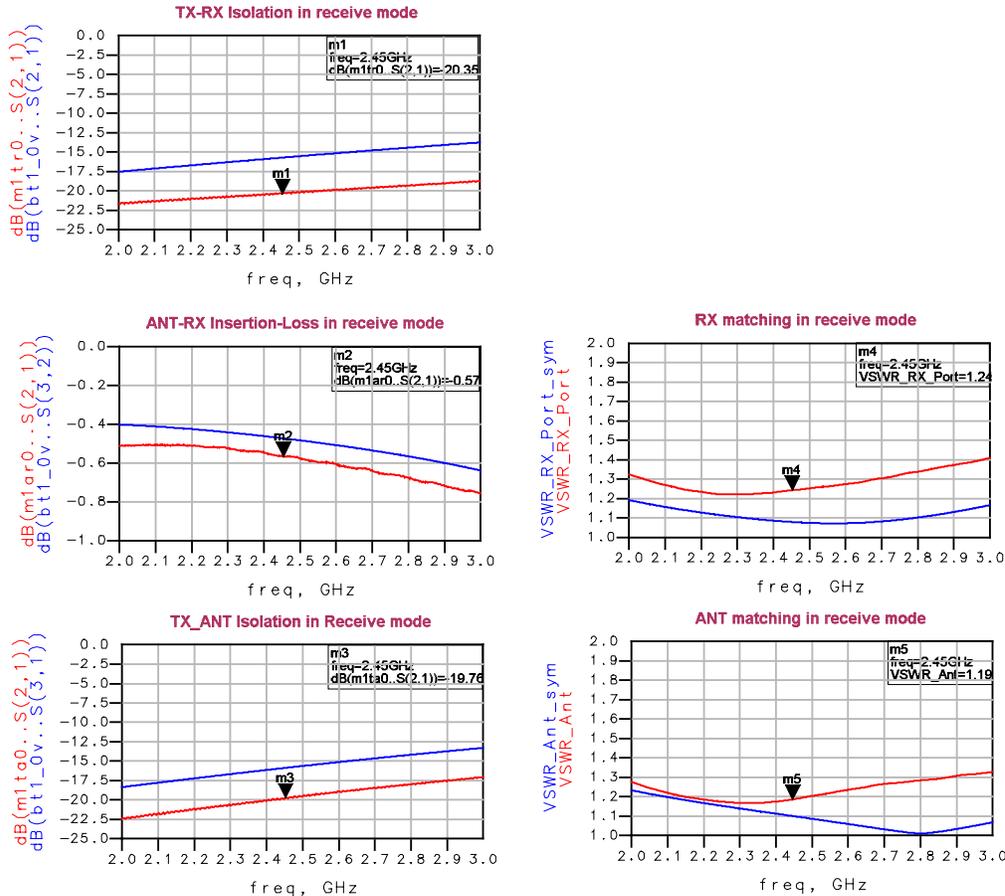


Figure 10; Results in RX mode; red curves are measurements, blue curves are the simulated ones

Remark: Loss and Isolation results are all including approximately 0.2 dB loss of the SMA connectors which were used to feed the RF signals through the design. this has a great effect on the Insertion-Loss results.

Recommendations.

- 1 In this design the BAP51-02 was used because it's designed for switching applications related to Insertion Loss and Isolation. When for instance a better IM distortion is recommended it's better to use the BAP64-02 of Philips Semiconductors.
- 2 As you can see the $\lambda/4$ section still needs a lot of boards space. This section could be replaced by a lumped element configuration, which results in an extra boardspace reduction.

References:

- 1; Gerald Hiller, "Design with PIN diodes", App note APN1002 Alpha industries inc.
- 2; Gerald Hiller, "Predict intercept points in PIN diode switches", Microwaves & RF, Dec. 1985.
- 3; Robert Caverly and Gerald Hiller, "Distortion in PIN diode control circuits" IEEE Trans.Microwave theory tech.,May 1987.